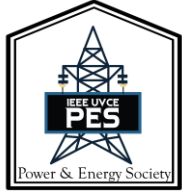


VOLTORB - SEPTEMBER

Digital Clock

Problem statement



Eddie, Norby and Veeko kidnapped Baby Bink, and we all know how that ended. In short, their venture landed them in prison. In order to escape from prison, they need a bunch of supplies. They have a chisel and a tool set, they have food and water in case it takes too long. The only hurdle is in escaping the guard outside. They cannot see where the guard is from inside. But they have outside information that the guard takes a nap at time x (you can choose the time). Unfortunately for them, there is no way of knowing what time it is. Build a digital clock using ICs and other necessary components, and help the inmates keep track of time.

Instructions:

1. Usage of microcontroller is NOT allowed.
2. The clock has to be precise to minutes. You can choose the 12-hour or 24-hour format.
3. The time has to be displayed in hexadecimal system.

STEPS

Pulse generation

This can be done using a 555-timer IC in astable mode.

Mod-60 counter

To count up to 60 minutes. We start from minutes because that is the problem requirement.

Mod-12/Mod-24 counter

The question gives us the liberty to choose the format.

GANG MEMBERS


**Pulse
generator**

**Binary
Counter**

**7-segment
display**

**7-segment
display
decoder/driver**


**Basic Logic
gates**

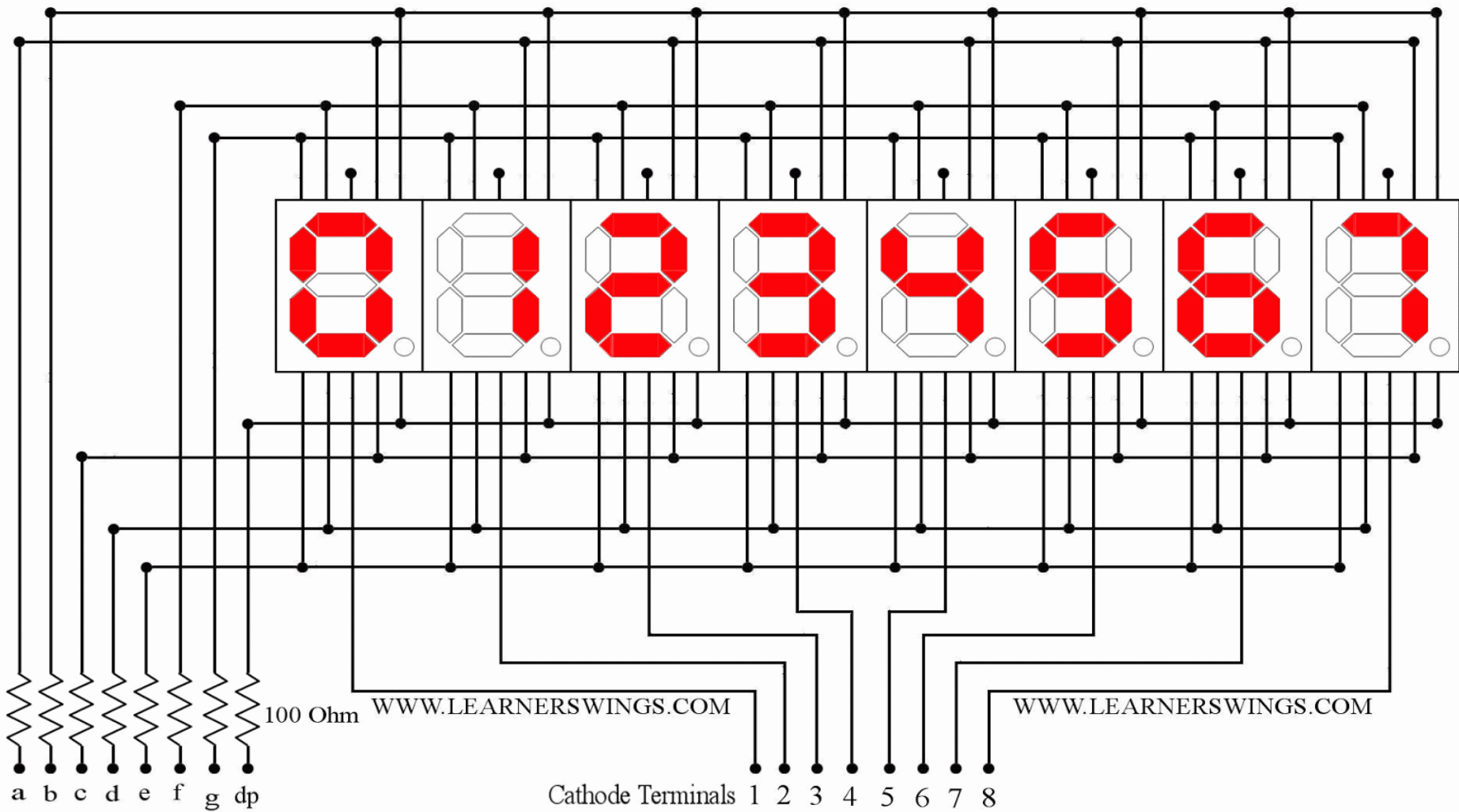

Pulse generation

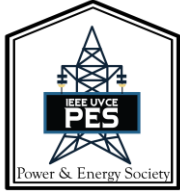This can be done using a 555-timer IC in astable mode.





Mod-60 counter

We need a counter that counts from 0-59 for the minutes section, so we use a combination of mod-10 and mod-6 counter here.

Mod-12 counter

For the hours section. A mod-12 counter counts from 0-11 and starts over.

If you choose to use the 24-hour format, you would have to use a mod-24 counter instead.



7-segment: decoder, driver and display

The 7-segment display is used for displaying digits.

Multiple ICs such as 4026, 4511 etc can be used as decoder/driver. The purpose of these is to decode the binary input from the counter into decimal and drive the 7-segment display to display the decimal number.



**Put it all
together.**

Worked, didn't it?

No? Check connections,
check IC inputs and
outputs.

Still no? Try using a
replacement IC/different
method of pulse
generation.

**How would you do the same
with a microcontroller?**







IT IS NOW COMPLETE.

Eddie, Norby and Veeko have been successful in their prison break.

Baby Bink better be on a lookout!

